

Dear Rev. Burbatis,

Thank you very much for your most complimentary letter and the attached literature you sent me. Unfortunately, and for some time to come, I will not be able to purchase your books.

In order to reciprocate, I send attached the schematics of a radionic device that I designed but could not build due to the high cost of the elements here. I drew it after reading the book "The Secret of Tesla" by the American researcher Thomas L. Bearden, the books of Dr. Walter Russell and the works of Dr. Wilhelm Reich. As I could not build and experiment the apparatus I thought that it would be a good idea to release its design so that whosoever is financially endowed can build one for him/herself.

Again, thanking you for your kindness, I remain,

Sincerely yours,

Jorge Resines
Jorge Resines

Republic of Argentina

TRANSISTORIZED SEMI-AUTOMATIC RADIONIC DEVICE FOR DIAGNOSIS

AND HEALING.

a) List of Parts:

C1 to C10: Variable condensers, of 3⁶5 PFD each.
C11: 0.047 uF electrolytic (oil) condenser
C12: 500 uF electrolytic (oil) condenser x 25 volts
C13: 1 uF electrolytic (oil) condenser or two 0.047 uF electrolytic (oil) condensers in parallel.
R1: Fixed resistor, 40 Kilohms. (Carbon resistor)
R2: Wirewound resistor, 2 ohms, 10 watts.
R3: Fixed resistor, 50 ohms, 10 watts. (Carbon resistor)
TRI: TIP 32 A transistor, or similars.
D1: Silicon Diode, 1 Ampere, BY 127 or similars.
T1: Filament transformer, 6 volts, 0.15 Ampere.
V: Voltmeter
T2: Transformer, Primary A.C. line, Secondary: 9 volts, 1 Ampere.
FB: Television Fly-Back. ✓
PS: A.C. socket. ✓
GE NE-83: Neon Bulb.
D.P. : Detector Plate, a common copper foil sheet of 15 cms. x 15 cms.
SCR: Silicon Controlled Rectifier, GE C7B or similars.

b) Mode of operation:

Those who are acquainted with the field of Radionics, know that it is necessary for the operator to have a certain psychic sensibility in order to "tune" the disease rate and the counter-rate that will eliminate said disease. This circuit does away with such requisite, because it uses the capacity of the human body in order to tune the disease rate. The patient is sitting on a chair, and the Detector Plate is placed on the diseased, or infected, zone. The A.C. power is connected and the operator begins to tune C1 until the Light Bulb - not shown - plugged at P.S. lights; afterwards, and in a similar fashion the operator tunes C2, C3,, until C10 is tuned. After this is done, the Voltmeter and the Tesla Coil output are switched on. The Output of the Tesla Coil is radiated, by means of a mono-electrode lamp like the one patented by Dr. Tesla (see U.S. Patents Nos. 454,622 and 455,069) which light can be filtered through an artificial emerald for a better result. The Output should be radiated on the head of the patient, because the high-frequency energy, modulated by the tuned variable condensers, is the equal opposite of the energy that has caused the disease. And, as happens in magnetism, opposite polarities cancel each other and the disease is eliminated. The tuning of the condensers will have to be changed when the inten-

sity of the disease diminishes. Due to the polarity of the different zones of the body, the best course of action is to radiate the Output on the head, so that the body may absorb it and because the energy will be attracted by the specific radiation of the diseased zone there is no danger that the disease may spread to other zones of the body.

Suggested usage is as follows: When tuning the disease - in the beginning - move all variable condensers from left ~~to~~ right until the maximum brilliance of the Light Bulb - or maximum voltage in the connected Voltmeter - is attained. You must do so beginning with C1 and ending with C10. Once this is done proceed to radiate the output over the head of the patient. When resonance is lost due to the beginning of the healing, move C10 from right to left until the Voltmeter or the Light Bulb show maximum. If C10 marks zero, then move C9 counterclockwise until maximum is attained; if C9 does not respond, proceed to move C8 and so on downwards. When all variable condensers mark zero (0), then the disease is healed.

